

--	--	--	--	--	--	--	--	--	--

MULTIMEDIA UNIVERSITY

FINAL EXAMINATION

TRIMESTER 2, 2017/2018

EEN1046 – ELECTRONICS III
(TE, RE, BE)

6 MARCH 2018
2:30 p.m. - 4:30 p.m.
(2 Hours)

INSTRUCTIONS TO STUDENTS

- (a) This booklet consists of 6 pages including cover pages with 4 questions only.
- (b) Attempt **ALL** questions given. All questions carry equal marks and distribution of the marks for each question is given.
- (c) Please write all your answers in the Answer Booklet provided.
- (d) All necessary working **MUST** be shown.

Question 1

- (a) Sketch a symbol diagram of an op-amp and name all the input/output ports. [5 marks]

- (b) Given the op-amp configuration in Figure Q1 (b) below, determine the value of R_f required to produce a closed loop voltage gain of -150 . What type (inverting or non-inverting) of op-amp is this? [5 marks]

 


Figure Q1 (b)

- (c) Given the summing amplifier in Figure Q1 (c) with $R_F = 20 \text{ k}\Omega$, $R_1 = 2 \text{ k}\Omega$, $R_2 = 4 \text{ k}\Omega$, and $R_3 = 6 \text{ k}\Omega$.
- Determine the type (inverting or non-inverting) of the summing amplifier in Figure Q1 (c) and justify your answer. [2 marks]
 - Express the output voltage, v_o , in terms of v_{I1} , v_{I2} , and v_{I3} . [6 marks]
 - Determine the output voltage, v_o , given the v_{I1} is 2 V, v_{I2} is 4 V, and $v_{I3} = 6 \text{ V}$. [3 marks]
 - Modify the circuit components values so that the summing amplifier in Figure Q1 (c) gives $v_o = -(v_{I1} + v_{I2} + v_{I3})$. [4 marks]

 


Figure Q1 (c)

Continued ...

Question 2

- (a) Figure Q2 (a) shows a Band-Pass filter circuit with constant pass-band gains. Given $R_1=R_1'=R_F=R_F'=10\text{k}\Omega$, $C=10\text{nF}$, $R=10\text{k}\Omega$, $C'=5\text{nF}$, $R'=12\text{k}\Omega$ and Bandwidth, $BW=1\text{ kHz}$.

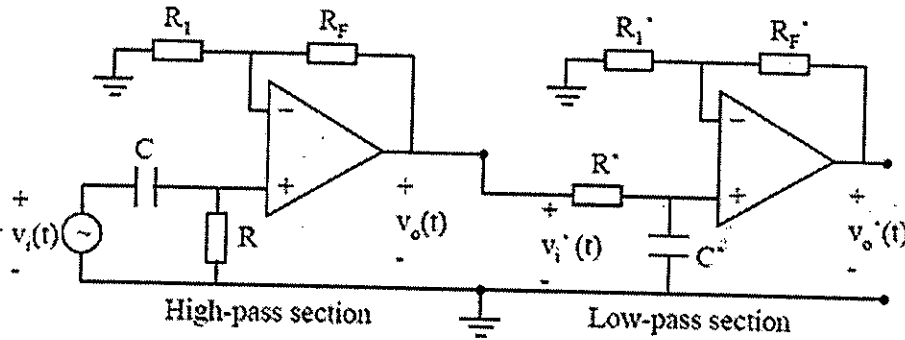


Figure Q2 (a)

- Calculate the high pass gain, K_{HP} and low pass gain, K_{LP} . [2 marks]
 - Calculate the overall band pass gain, K_{BP} . [2 marks]
 - Calculate the highest cutoff frequency, f_H and lower cutoff frequency, f_L . [2 marks]
 - Calculate the quality factor Q . [2 marks]
- (b) The Darlington-pass transistor regulator circuit shown in Figure Q2 (b) regulates the output voltage to 5V. Given that the transistor current gain for Q_1 and Q_2 are 100 and $V_{BE} = 0.7\text{V}$.
- Determine the total Darlington-pair current gain, h_{FE} . [1 mark]
 - Calculate the Zener voltage, V_Z and Zener current I_Z . [6 marks]

 


Figure Q2 (b)

Continued ...

(c)

(i) What is the difference between sawtooth and triangular waveforms? [2 marks]

(ii) Design a triangular wave generator, as shown in Figure Q2 (c), for an amplitude voltage of $\pm 10\text{V}$ and oscillation frequency of 10KHz . Assume $V_{CC} = \pm 15\text{V}$, $C = 1\text{nF}$. Assume $R_1 = 1\text{k}\Omega$. [6 marks]

(iii) Modify the circuit to produce a sawtooth waveform instead of triangular waveform. [2 marks]

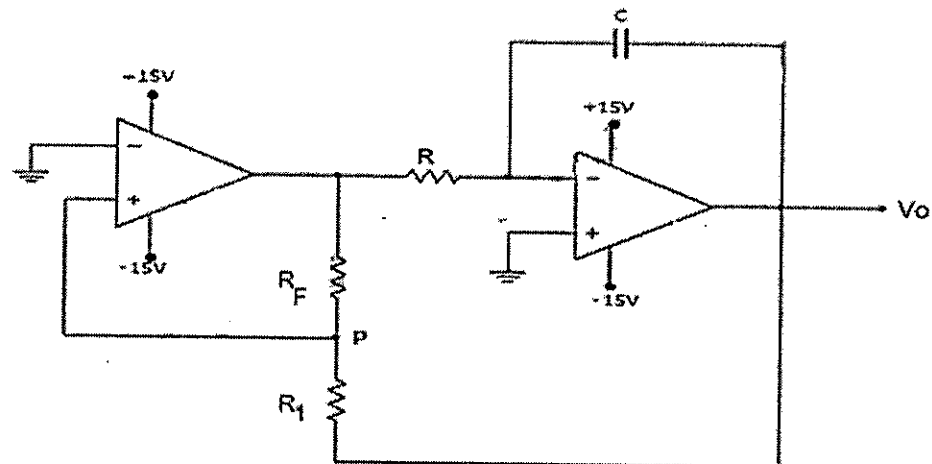


Figure Q2 (c)

Question 3

(a) The op-amp in Figure Q3 has the following property obtained from datasheet:

 


Figure Q3

Continued ...

Parameters	Conditions	Min	Typ	Max	Units
Input Offset Voltage	$T_A = 25^\circ C$		1.0	3.0	mV
Input Offset Current	$T_A = 25^\circ C$		3.0	30	nA
Input Bias Current	$T_A = 25^\circ C$		15	80	nA
Input offset voltage drift coefficient	D_v			15	$\mu V/^\circ C$
Input offset current drift coefficient	D_i			0.5	$nA/^\circ C$
Input bias current drift coefficient	D_b			0.5	$nA/^\circ C$
Power Supply Rejection Ratio	PSRR	75	85		dB

- (i) Determine the drift output offset voltage of the circuit in Figure Q3 at temperature $T = 45^\circ C$. [7 marks]
- (ii) Determine maximum output offset voltage due to V_{IO} , for an operating temperature of $45^\circ C$. Assuming $I_{IO} = I_B = 0$. [3 marks]
- (iii) Determine the maximum output offset voltage due to V_{IO} , at room temperature ($25^\circ C$). Assuming $I_{IO} = I_B = 0$. [3 marks]
- (iv) Determine the maximum output offset voltage, taking into account the effect of all the relevant dc offset value, for an operating temperature of $45^\circ C$. [3 marks]
- (b) Stability is a very important consideration when using op-amps. Discuss the stability in op-amp while performing positive feedback and negative feedback respectively. [9 marks]

Question 4

- (a) A temperature sensor senses a temperature ranging from 0° to $20^\circ C$ and output a corresponding voltage of from $-5V$ to $+5V$. The output voltage linearly increases with the temperature sensed. Design a Schmitt trigger circuit that will turn on a heater (Schmitt trigger output = $+V_{sat}$) when the temperature drops below $5^\circ C$ and turn off the heater (Schmitt trigger output = $-V_{sat}$) when temperature rises above $15^\circ C$. Assume supply voltage $V_{cc} = \pm 12V$ and $V_{sat} = V_{cc} - 1$. Assume diode voltage of $0.7V$ in your design.
- (i) What type of Schmitt trigger circuit is required in this sensing circuit? Justify your answer. [2 marks]
- (ii) Sketch and label the Schmitt trigger circuit. [3 marks]
- (iii) Sketch the output of the Schmitt trigger circuit in relation to the sensing input of the temperature sensor. [3 marks]
- (iv) Evaluate the analysis on the design in order to determine the resistive components values required for the Schmitt trigger circuit. [5 marks]

Continued ...

- (b) Assuming an ideal diode D as shown in Figure Q4 (b), a voltage V_{in} is connected to the inverting input of a precision clamper circuit.

 


Figure Q4 (b)

- (i) If the input voltage $V_{in} = V_m \sin \omega t$, explain briefly the operation of the circuit and evaluate the output voltage, V_o from 0 to 2π time intervals.

[7 marks]

- (ii) The input voltage, $V_{in} = 2 \sin \omega t$ is to be clamped to a DC level of +8V. Assuming an ideal op-amp and $\pm 12V$ supply voltage, modify the circuit in Figure Q4 (b) to obtain the required output.

[5 marks]

End of Page